

Physics 30 - Lesson 22A
AC Power

1) $V_{eff} = 240V$ ✓
 /5 $R = 3200\Omega$ ✓
 $I_{max} = ?$

$$I_{eff} = \frac{V_{eff}}{R} = \frac{240V}{3200\Omega} = 0.075A$$

$$I_{max} = \frac{I_{eff}}{0.707} = \frac{0.075A}{0.707} = \boxed{0.11A}$$

2) $V_{max} = 180V$ ✓
 /4 $R = 220\Omega$

$$I_{max} = \frac{V_{max}}{R} = \frac{180V}{220\Omega} = 0.818A$$

$$I_{eff} = I_{max} \cdot 0.707 = (0.818A)(0.707)$$

$$\boxed{I_{eff} = 0.578A}$$

3) $V_{Rms} = 120V$ ✓
 /3 $P = 60W$ ✓
 $R = ?$

$$R = \frac{V^2}{P} = \frac{(120V)^2}{60W} = \boxed{240\Omega}$$

4) $I_{max} = 3.0V$ ✓
 /4 $P = 1000W$ ✓
 $V_{Rms} = ?$

$$V_{Rms} = \frac{P}{I_{Rms}} = \frac{P}{I_{max} (0.707)} = \frac{1000W}{3.0(0.707)}$$

$$\boxed{V_{Rms} = 4.7 \times 10^2 V}$$

5) $P_{Avg} = 100W$ ✓
 /2 $P_{max} = ?$

$$P_{max} = 2 \times P_{Avg} = 2(100W)$$

$$\boxed{P_{max} = 200W}$$

6) $R = 15\Omega$ ✓
 $V_{eff} = 240V$ ✓
 /6 $P = ?$ ✓
 $P_{max} = ?$ ✓
 $P_{min} = ?$ ✓

$$P_{Avg} = \frac{V^2}{R} = \frac{(240V)^2}{15\Omega} = \boxed{3.8 \times 10^3 W}$$

$$P_{max} = 2 \times 3.8 \times 10^3 = \boxed{7.7kW}$$

$$\boxed{P_{min} = 0}$$

7) $f = 60Hz$ ✓
 /2 $vibrations = \frac{60}{s} \times \frac{60s}{min} \times \frac{60min}{hr} \times \frac{24hr}{day}$ ✓
 $vibrations = 5.184 \times 10^6 Hz = \boxed{5.184MHz}$ ✓

8) $V_{\max} = 65V$ ✓
 $I_{\text{rms}} = ?$
 $R = 25\Omega$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{R} = \frac{V_{\max}(0.707)}{R} = \frac{65V(0.707)}{25\Omega} \checkmark$$


$$I_{\text{rms}} = 1.8A \checkmark$$

9) $V = 120V$
 $I_{BD} = 11A$ ✓
 $I_{VC} = 4.0A$
 $t_{BD} = 0.25h$
 $t_{VC} = 0.50h$

a) BD $P_{BD} = V \cdot I_{BD} = 120V(11A) \checkmark$
 $P_{BD} = 1.3kW \checkmark$

b) VC $P_{VC} = V \cdot I_{VC} = 120V(4.0A) \checkmark$
 $P_{VC} = 0.48kW \checkmark$

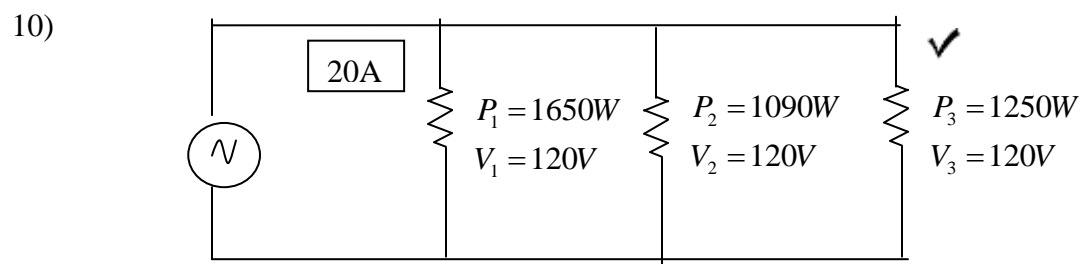c) $\frac{E_{BD}}{E_{VC}} = \frac{P_{BD}(t_{BD})}{P_{VC}(t_{VC})} = \frac{(1.3kW)(0.25h)}{(0.48kW)(0.5h)} \checkmark$
 $\frac{E_{BD}}{E_{VC}} = \frac{1.4}{1} \checkmark$



/12

a) Toaster $R = \frac{V^2}{P} = \frac{(120V)^2}{1650W} = 8.73\Omega \checkmark$

Iron $R = \frac{V^2}{P} = \frac{(120V)^2}{1090W} = 13.2\Omega \checkmark$

Microwave $R = \frac{V^2}{P} = \frac{(120V)^2}{1250W} = 11.52\Omega \checkmark$

$$\frac{1}{R_T} = \frac{1}{8.73} + \frac{1}{13.2} + \frac{1}{11.51} \checkmark$$

$$R_T = 3.61\Omega \checkmark$$

b) $I = \frac{V}{R} = \frac{120V}{3.61\Omega} = 33.3A \checkmark$
 circuit breaker "opens" ✓

Transformers

11) $\frac{N_p}{N_s} = \frac{V_p}{V_s}$ ✓
 /3 $\frac{13}{1} = \frac{120V}{V_s}$ ✓ $V_s = \frac{120}{13} = \boxed{9.23V}$ ✓

12) $V_p = 120.0V$ ✓
 /4 $V_s = 4150V$ ✓
 $N_p = 17$ ✓ $N_s = ?$
 $N_s = \frac{N_p N_s}{V_p} = \frac{17(4150V)}{120.0V}$ ✓
 $\boxed{N_s = 588 \text{ turns}}$ ✓

13) $V_p = 120.0V$ ✓
 /4 $V_s = 10.0V$ ✓
 $N_p / N_s = ?$
 $\frac{N_p}{N_s} = \frac{V_p}{V_s} = \frac{120V}{10.0V} = \frac{12}{1}$ ✓
 $\boxed{\text{ratio is 12 to 1}}$ ✓

14) $I_s = 3.4A$ ✓
 $I_p = ?$ ✓
 /4 $\frac{N_p}{N_s} = \frac{8}{1}$ ✓
 $\frac{I_s}{I_p} = \frac{N_p}{N_s}$ ✓
 $I_p = \frac{I_s N_s}{N_p} = \frac{3.4A(1)}{8}$ ✓
 $\boxed{I_p = 0.43A}$ ✓

15) $I_s = 0.10A$ ✓
 $V_p = 120V$ ✓
 $P = 60.0W$ ✓
 /7 a) $P = I_s V_s$ ✓
 $V_s = \frac{P}{I_s} = \frac{60.0W}{0.10A}$ ✓
 $\boxed{V_s = 6.0 \times 10^2 V}$ ✓
 b) step up transformer ✓
 $\frac{N_p}{N_s} = \frac{V_p}{V_s} = \frac{120V}{600V} = \frac{1}{5}$ ✓
 $\boxed{\text{ratio is 1 to 5}}$ ✓

16) $\frac{N_p}{N_s} = \frac{1}{43}$ Find V_s or I_p
 $V_p = 120V$ ✓
 $I_s = 1.5 \times 10^{-3} A$
 /7 $P = ?$

$$\frac{V_s}{V_p} = \frac{N_s}{N_p}$$

$$V_s = \frac{N_s}{N_p} \times V_p$$
 ✓
$$V_s = \frac{43}{1} \times 120V$$
 ✓
$$V_s = 5.2 \times 10^3 V$$
 ✓
$$P = I_s V_s = 1.5 \times 10^{-3} \times 5.2 \times 10^3$$
 ✓
$$\boxed{P = 7.7W}$$
 ✓

17) $P = 1.2 \times 10^6 W$ ✓
 $R = 7.0 km \times 2 lines \times 5.0 \times 10^{-2} \Omega / km$
 $R = 0.70 \Omega$ ✓
 $V = 1200V$


/12

a) $I = \frac{P}{V} = \frac{1.2 \times 10^6 W}{1200V}$ ✓
 $I = 1000A$ ✓
 $P_{loss} = RI^2 = 0.70 \Omega (1000A)^2$ ✓
 $\boxed{P_{loss} = 7.0 \times 10^5 W}$ ✓

b) $\frac{V_s}{V_p} = \frac{N_s}{N_p}$ ✓
 $V_s = \frac{N_s V_p}{N_p} = \frac{100(1200V)}{1} = 120000V$ ✓
 $I = \frac{P}{V} = \frac{1.2 \times 10^6 W}{1.2 \times 10^5 W}$ ✓
 $I = 10A$ ✓
 $P_{loss} = I^2 R = (10A)^2 (0.70 \Omega)$ ✓
 $\boxed{P_{loss} = 70W}$ ✓

- 18)
- /3
1. Electrical energy is transmitted much more efficiently with high voltage / low current ✓
 2. Transformers can be used to produce the high voltage ✓
 3. Transformers work on AC, not DC ✓
-

19)

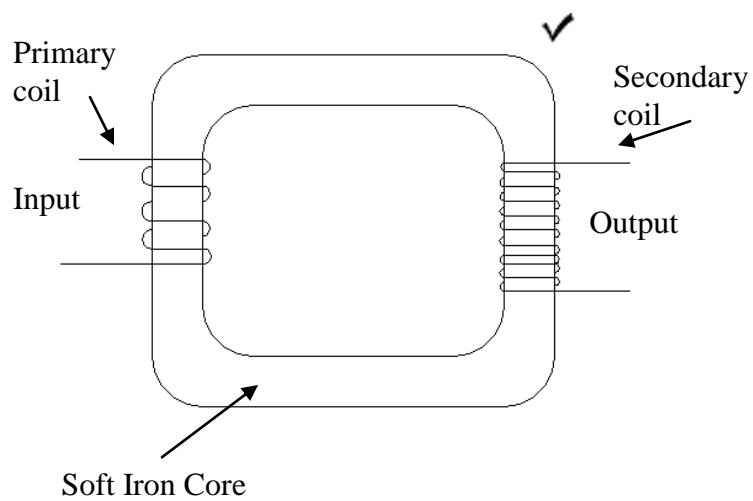

/4

Primary coil ✓

- AC current induces a changing magnetic field

Iron core ✓

- connects the changing magnetic field to the secondary coil

Secondary Coil ✓

- the changing magnetic field induces a new alternating current in the coil

20)

4KV → 240V ✓

/1